

# Verilog Tutorial

# Hardware Description Languages


- Verilog:
  - Simple C-like syntax for structural and behavior hardware constructs
  - Mature set of commercial tools for synthesis and simulation
  - **Used in this course!**
- VHDL:
  - Semantically very close to Verilog
  - More syntactic overhead
  - Extensive type system for “synthesis time” checking
- System Verilog:
  - Enhances Verilog with strong typing along with other additions

# Verilog: Brief History

- Developed by Gateway in 1985, acquired by Cadence in 1989.
- Originally for simulation; synthesis support came later.
- Released publicly in 1990 to compete with VHDL (developed by the US Department of Defense).
- Became popular in Silicon Valley due to strong tool support and C-like syntax.
- VHDL is still popular within the government, in Europe and Japan, and some universities.
- Most major CAD frameworks now support both.
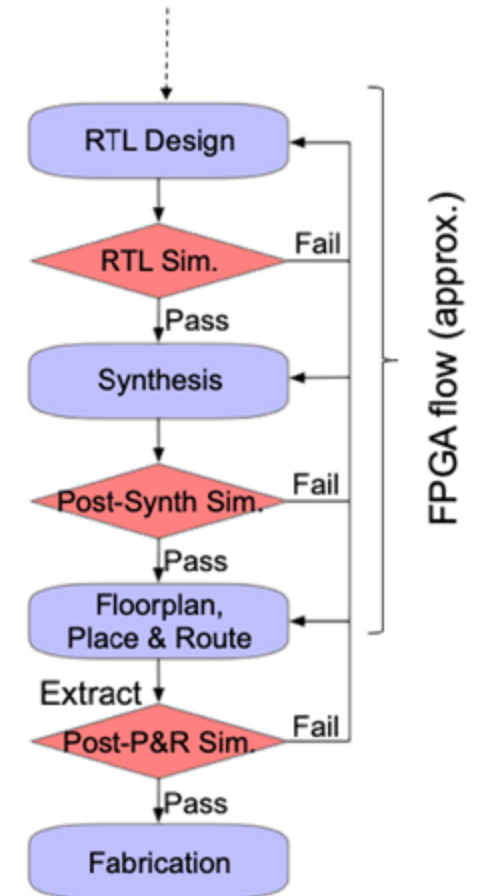
# Logic Synthesis

- Verilog and VHDL started out as simulation languages but soon programs were written to automatically convert Verilog code into low-level circuit descriptions (netlists).
- Synthesis converts Verilog (or other HDL) descriptions to an implementation using technology-specific primitives:
  - For FPGA: LUTs, FlipFlops, and BRAMs.
  - For ASICs: standard cells and memory macros.



# Agenda

- Combinational Circuits
  - Assign statement
  - Always blocks
    - Case statement
  - Generator
- Sequential Circuits
  - Latches and FlipFlops
  - Always block
    - Sensitivity list
  - Blocking vs Nonblocking

# Verilog Introduction


- Modules define components in a circuit.
- Two ways to describe modules:
  - Structural Verilog:
    - Defines sub-components and connections (text-based schematic).
    - Precise control but tedious to write and read.
    - Needed for FPGA/ASIC mapping.
  - Behavioral Verilog:
    - Describes what a component does, not how.
    - Easier to write but depends on synthesis tools.
- Modular Design:
  - Hierarchical structure with a top-level module as the full design or testbench.

# Combinational Logic

- Output is a function of only the current inputs.
- No memory or state involved.
- The same inputs always produce the same outputs.
- No clock required—outputs update immediately with input changes.
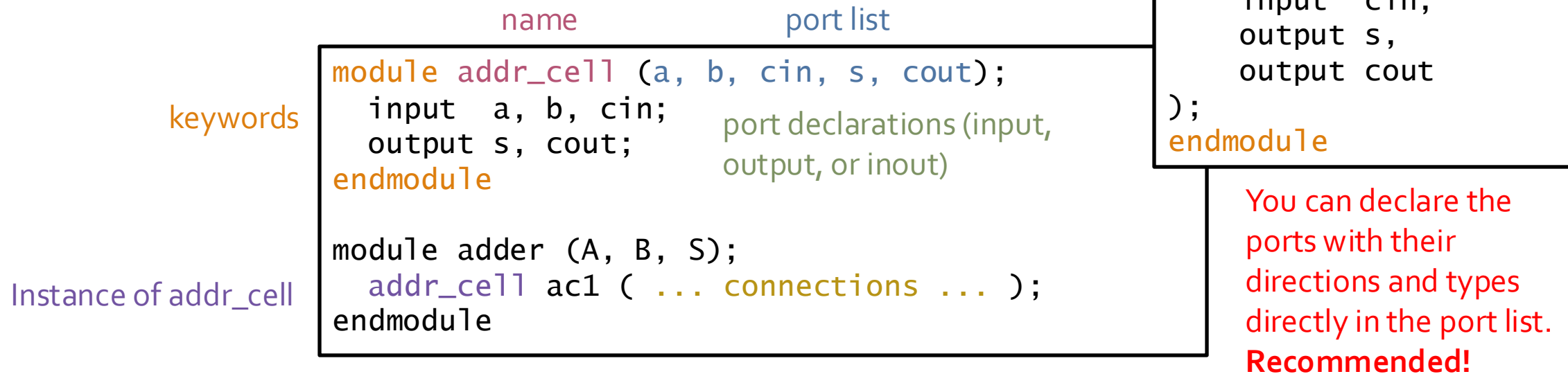
# Verilog Modules and Instantiation

- Modules define circuit components.
- Instantiation defines hierarchy of the design.




Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.



# Structural Model – 1-bit Adder Example

```
module add_cell(  
    input  a,  
    input  b,  
    input  cin,  
    output s,  
    output cout  
);  
  
    wire w1, w2, w3;  
  
    xor g1 (w1, a, b);  
    xor g2 (s, w1, cin);  
  
    and g3 (w2, a, b);  
    and g4 (w3, w1, cin);  
  
    or  g5 (cout, w2, w3);  
  
endmodule
```

Build-in gates!

 

## Notes:

- The instantiated gates are not “executed”. They are active always.
- Undeclared variables assumed to be wires. Don’t let this happen to you!

# Simple Behavioral Model


```
module foo (  
    input in1,  
    input in2,  
    output out  
);  
  
    assign out = in1 & in2;  
  
endmodule
```

**“continuous assignment”**  
Connects out to be the  
logical “and” of in1 and in2.

- Short-hand for explicit instantiation of bit-wise “and” gate (in this case).
- The assignment continuously happens, therefore any change on the rhs is reflected in out immediately
- Not like an assignment in C that takes place when the program counter gets to that place in the program.

# Behavioral Model – 1-bit Adder Example

```
module addr_cell(  
    input a,  
    input b,  
    input cin,  
    output s,  
    output cout  
);  
  
    wire w1, w2, w3;  
  
    assign w1 = a ^ b;  
    assign s = w1 ^ cin;  
    assign w2 = a & b;  
    assign w3 = w1 & cin;  
    assign cout = w2 | w3;  
  
endmodule
```

 

# Even Simpler!

```
module addr_cell(  
    input  a,  
    input  b,  
    input  cin,  
    output s,  
    output cout  
);  
  
    assign {cout, s} = a + b + cin;  
  
endmodule
```

# Instantiation, Signal Array, Named ports

- Example: 4-bit Ripple-Carry Adder.
  - $S[4:0] = A + B$  (5-bit sum)

```
module adder4 (  
    input  [3:0] A, Signal array. Declares A[3], A[2], A[1], A[0]  
    input  [3:0] B,  
    output [4:0] S  
);  
  
    wire c1, c2, c3;  
  
    Named ports. Highly recommended. → prevent errors if port order changes.  
    addr_cell ac0 (.a(A[0]), .b(B[0]), .cin(1'b0), .s(S[0]), .cout(c1));  
    addr_cell ac1 (.a(A[1]), .b(B[1]), .cin(c1), .s(S[1]), .cout(c2));  
    addr_cell ac2 (.a(A[2]), .b(B[2]), .cin(c2), .s(S[2]), .cout(c3));  
    addr_cell ac3 (.a(A[3]), .b(B[3]), .cin(c3), .s(S[3]), .cout(S[4]));  
  
endmodule
```

# Verilog Operators

Verilog Operator	Name	Functional Group
[ ]	bit-select or part-select	
( )	parenthesis	
!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
~^ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{ { } }	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic

<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	case equality	equality
!=	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
?:	conditional	conditional

# Continuous Assignment Examples

- Assign values whenever there is a change in the RHS.
- Model combinational logic without specifying an interconnection of gates.

```
assign R = X | (Y & ~Z);  
assign r = &X;  
assign R = (a == 1'b0) ? X : Y;  
assign P = 8'hff;  
assign P = X * Y;  
assign P[7:0] = {4{X[3]}, X[3:0]};  
assign {cout, R} = X + Y + cin;  
assign Y = A << 2;  
assign Y = {A[1], A[0], 1'b0, 1'b0};
```

```
wire [3:0] A, X, Y, R, Z;  
wire [7:0] P;  
wire r, a, cout, cin;
```

# Non-Continuous Assignments

- A bit unusual from a hardware specification point of view.
- Shows off Verilog roots as a simulation language.

“reg” type declaration. Not really a register in this case. Just a Verilog idiosyncrasy.

brackets multiple statements (not necessary in this example).

```
module and_or_gate (  
    input  in1,  
    input  in2,  
    input  in3,  
    output reg out  
);  
    always @(in1 or in2 or in3) begin  
        out = (in1 & in2) | in3;  
    end  
  
endmodule
```

Sensitivity list,  
triggers the action in the body



# Styles of doing combo logic

## Assign 'Explicit Style'

```
wire empty;
```

```
assign empty = (cnt==0) && !wr_val;
```

```
reg [ST_W-1:0] state;  
wire [ST_W-1:0]. state_nxt;
```

```
assign state_nxt = val_1_in ? ACCEPT_ST :  
                    val_2_in ? WAIT_ST :  
                    state ;
```

## Always @(\*) 'Serial Style'

```
reg empty;
```

```
always @(*) begin  
    empty = (cnt==0) && !wr_val;  
end
```

```
reg [ST_W-1:0] state, state_next;
```

```
always @(*) begin  
    state_next = state; //default  
    if (val_1_in)  
        state_next = ACCEPT_ST;  
    else if (val_2_in)  
        state_next = WAIT_ST;  
end
```

# Always Blocks

- Always blocks give us some constructs that are impossible or awkward in continuous assignments.

The statement(s) corresponding to whichever constant matches "select" get applied.

```
module mux4 (  
    input  in0,  
    input  in1,  
    input  in2,  
    input  in3,  
    input  [1:0] select,  
    output reg out  
);  
    always @ (in0 or in1 or in2 or in3 or select) begin  
        case (select)  
            2'b00: out = in0;  
            2'b01: out = in1;  
            2'b10: out = in2;  
            2'b11: out = in3;  
        endcase  
    end  
endmodule // mux4
```

Couldn't we just do this with nested "if"s? Well yes and no!

# Always Blocks

Nested if structure leads to “priority logic” structure:  
with different delays for different inputs  
(in3 to out delay > than in0 to out delay).  
Case version treats all inputs the same.

- Nested if-else example:

```
module mux4 (  
    input  in0,  
    input  in1,  
    input  in2,  
    input  in3,  
    input  [1:0] select,  
    output reg out  
);  
    always @ (in0 or in1 or in2 or in3 or select) begin  
        if (select == 2'b00)  
            out = in0;  
        else if (select == 2'b01)  
            out = in1;  
        else if (select == 2'b10)  
            out = in2;  
        else  
            out = in3;  
    end  
endmodule // mux4
```

# Generate

```
adder #(.N(64)) adder64 ( ... );
```

Overwrite parameter N at instantiation.


```
module adder (  
    parameter N = 4;  
    input  [N-1:0] A,  
    input  [N-1:0] B,  
    output [N:0] S  
);  
  
wire [N:0] carry;  
  
genvar i;  
generate  
    for (i = 0; i < N; i = i + 1) begin : bit  
        addr_cell ac (.a(A[i]), .b(B[i]), .cin(carry[i]), .s(S[i]), .cout(carry[i+1]));  
    end  
endgenerate  
  
assign carry[0] = 1'b0;  
assign S[N] = carry[N];  
  
endmodule
```

Declare a parameter with default value.  
Note: this is not a port. Acts like a "synthesis-time" constant.  
Replace all occurrences of "4" with "N".  
variable exists only in the specification - not in the final circuit.  
For-loop creates instances (with unique names)  
Keyword that denotes synthesis-time operations

- This is NOT a sequential for loop, this is just to replicate hardware! All in parallel!
- You can declare signals inside this scope
 
# Simplified Verilog Guidelines

- Combinational logic:
  - Continuous Assignment:  
`assign a = b & c;`
  - Always block with `@(*)`  
`always @(*) begin`  
    `a = b & c; // blocking statement`  
`end`



# Are these Combinational Circuits Correct?

```
always @(a or b) begin
    out = a + b + c;
end
```

```
assign out = in & out;
```

```
always @(*) begin
    case (addr[1:0]):
        2'd0: out = a;
        2'd1: out = b;
        2'd2: out = c;
    endcase
end
```

# Inside always blocks

## Case statements

BAD!!!

```
case (addr[1:0]):  
    2'd0: out = a;  
    2'd1: out = b;  
    2'd2: out = c;  
endcase
```

GOOD!

```
case (addr[1:0]):  
    2'd0: out = a;  
    2'd1: out = b;  
    2'd2: out = c;  
    2'd3: out = d;  
endcase
```

## Important notes:

- Used in **always** blocks
- A latch will be generated if *case* is not full and there is no default statement

GOOD TOO!

```
case (addr[1:0]):  
    2'd0: out = a;  
    2'd1: out = b;  
    2'd2: out = c;  
    default: out = d;  
endcase
```

# Agenda

- Combinational Circuits
  - Assign statement
  - Always blocks
    - Case statement
  - Generator
- Sequential Circuits
  - Latches and FlipFlops
  - Always block
    - Sensitivity list
  - Blocking vs Nonblocking




# Sequential Logic

- Output is a function of both the current inputs and the state.
- State represents the memory.
- State is a function of previous inputs.
- In synchronous digital systems, state is updated on each clock tick.

# Timing: Level vs. Edge


- Latch timing
- Flip-flop timing

 
 
# State Elements in Verilog

- Always blocks are the only way to specify the “behavior” of state elements.
- Synthesis tools will turn state element behaviors into state element instances.

```
module dff (  
    input d,  
    input clk,  
    input set,  
    input rst,  
    output reg q  
);  
  
    always @(posedge clk) begin  
        if (rst)  
            q <= 1'b0;  
        else if (set)  
            q <= 1'b1;  
        else  
            q <= d;  
    end  
endmodule
```



# The Sequential **always** Block

```
module comb(input a, b, sel,
            output reg out);

    always @(*) begin
        if (sel) out = b;
        else out = a;
    end

endmodule
```

```
module seq(input a, b, sel, clk,
            output reg out);

    always @(posedge clk) begin
        if (sel) out <= b;
        else out <= a;
    end

endmodule
```

# Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within always blocks, with subtly different behaviors.
- Blocking assignment (=): evaluation and assignment are immediate

```
always @(*) begin
    x = a | b;           // 1. evaluate a|b, assign result to x
    y = a ^ b ^ c;       // 2. evaluate a^b^c, assign result to y
    z = b & ~c;          // 3. evaluate b&(~c), assign result to z
end
```

- Nonblocking assignment (<=): all assignments deferred to end of simulation time step after all right-hand sides have been evaluated (even those in other active always blocks)

```
always @(*) begin
    x <= a | b;           // 1. evaluate a|b, but defer assignment to x
    y <= a ^ b ^ c;       // 2. evaluate a^b^c, but defer assignment to y
    z <= b & ~c;          // 3. evaluate b&(~c), but defer assignment to z
                        // 4. end of time step: assign new values to x, y, and z
end
```

# Combinational & Sequential

Use Nonblocking for Sequential Logic!

- **Blocking VS non-blocking** assignments

- `=` - blocking
- `<=` - non blocking, used only in `always@(posedge)` blocks

## Blocking

Statements inside `always` block are executed **serially** (like in software)  
**Order Matters!**

```
always @(*) begin
    b = a;
    c = b;
    d = b;
end
```

Is `d == a` ?

## Non Blocking

Statements inside `always` block are executed in **parallel**. Value assigned to LHS are taken from "previous cycle" values of RHS

```
always @(posedge clk) begin
    b <= a;
    c <= b;
    d <= b;
end
```

Is `d == a` ?

# Simplified Verilog Guidelines

- Combinational logic:

- Continuous Assignment:

`assign a = b & c;`

- Always block with `@(*)`

`always @(*) begin`

`a = b & c; // blocking statement`

`end`


- Sequential logic:

- Always block with `@(posedge clk)`

`always @(posedge clk) begin`

`a <= b & c; // nonblocking statement`

`end`

 

# Verilog in This Course

- We use behavioral modeling
- Favor continuous assign and avoid always blocks unless:
  - No other alternative: ex: state elements, case
  - Helps readability and clarity of code: ex: large nested if else
- Use named ports.
- Verilog is a big language. This is only an introduction.
  - Be careful about what you read on the web or hear from a chatbot. There are many bad examples out there.



# Verilog Tips

- Do not write C-code
  - Think hardware, not algorithms
    - Verilog is inherently parallel
    - Compilers don't map algorithms to circuits well
- Do describe hardware circuits
  - First draw a dataflow diagram
  - Then start coding

# Final Thoughts

- A large part of digital design is knowing how to write Verilog that gets you the desired circuit.
- First understand the circuit you want then figure out how to code it in Verilog.
- If you try to write Verilog without a clear idea of the desired circuit, you will struggle.

# Common Errors

- **No clock** signal or wrong **reset level**
- Combinational-logic If-else, case statements **without default case** (this will generate **latches**).
- **No initial values** for registers (which do require it)
  - [need to set the initial values in reset condition] for control registers
- Blocking assignment (=) in @(posedge clk) blocks, instead of (<=), when Flip-flops are intended

# Common Errors

- **Width mismatch on assignments between LHS and RHS**
- **Counter overflow/underflow**

# Common Errors

- **Multi-drive:** Try to assign different values to a same reg/wire

Wrong

```
always @(posedge clk)
begin
    if (rst)
        q <= 1'b0;
    if (en)
        q <= d;
end
```

Correct

```
always @(posedge clk)
begin
    if (rst)
        q <= 1'b0;
    else if (en)
        q <= d;
end
```